CPE 151 Digital IC Design

Project No.3

Daniel Komac

komacdan@hotmail.com

4/2/2020

Contents

S. No	Section	Page No.
1.	Ring Oscillator Schematic	5
2.	Ring Oscillator Test bench	6
3.	Ring Oscillator Test bench Waveform	7
4.	Ring Oscillator Layout	8
5.	Ring Oscillator DRC	9
6.	Ring Oscillator LVS	10
7.	Ring Oscillator Post-layout	12


Ring Oscillator

 $(W/L)_n = 1.8/.18$


 $(W/L)_p=3.6/0.18$

Using 180 nm Technology

Schematic (Ring Oscillator):

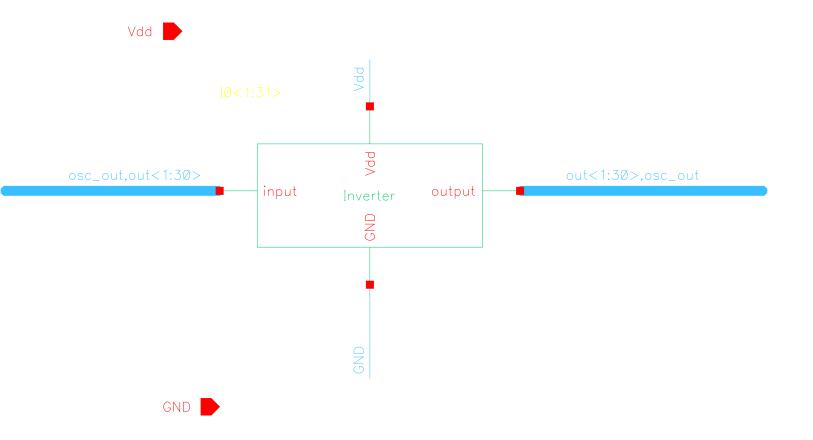

Test Bench (Ring Oscillator):

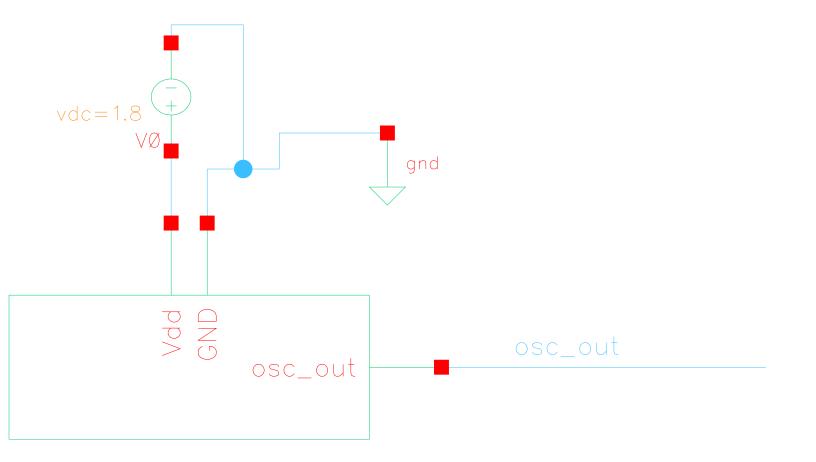


Test Bench Waveform (Ring Oscillator):

Transient Response

Thu Apr 2 14:14:29 2020



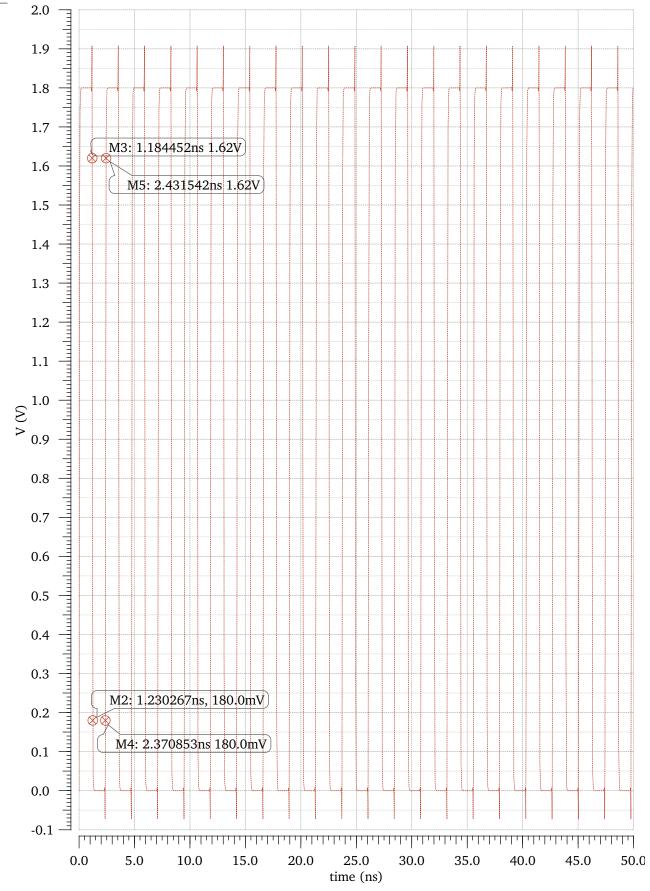


Layout (Ring Oscillator):

Г	1	

	II R I R	
	[
	Į.	

DRC (Ring Oscillator):

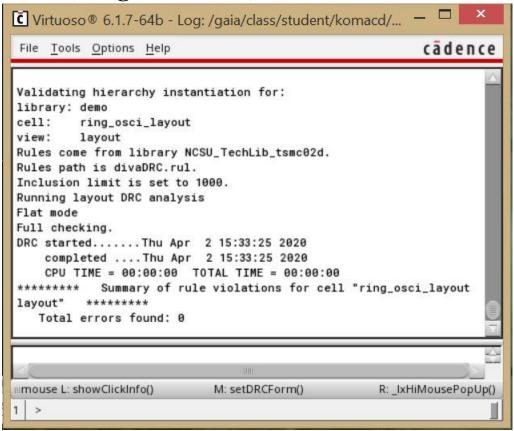

LVS (Ring Oscillator):

```
1: @(#)$CDS: LVS version 6.1.7-64b 09/27/2016 19:41 (sjfhw305) $
2:
 3: Command line: /software/cadence/installs/IC617/tools.lnx86/dfII/bin/64bit/LVS -dir /gaia/class/student/komacd/CadDemo/LVS -l -s -t /
    aia/class/student/komacd/CadDemo/LVS/layout /gaia/class/student/komacd/CadDemo/LVS/schematic
 4: Like matching is enabled.
 5: Net swapping is enabled.
 6: Using terminal names as correspondence points.
 7: Compiling Diva LVS rules...
8:
 9:
        Net-list summary for /qaia/class/student/komacd/CadDemo/LVS/layout/netlist
10:
            64
11:
                            nets
12:
            3
                            terminals
13:
            31
                            pmos
            31
14:
                            nmos
15:
16:
       Net-list summary for /qaia/class/student/komacd/CadDemo/LVS/schematic/netlist
17:
           count
18:
            33
                            nets
19:
            3
                            terminals
20:
            31
                            pmos
21:
            31
                            nmos
22:
23:
24:
        Terminal correspondence points
25:
        N61
                  N31
                            GND
26:
        N63
                  N32
                            Vdd
27:
        N62
                  N30
                            osc out
28:
29: Devices in the rules but not in the netlist:
30:
            cap nfet pfet nmos4 pmos4
31:
32:
        Ill-defined correspondence points.
33:
34:
        N62 N30 Accepted because one is a subset of the other
        N62 N30 Accepted because one is a subset of the other
35:
36:
37:
38:
            Device summary for layout
39:
                       bad total
40:
                         1
                               31
                nmos
41:
42:
43:
            Device summary for schematic
                       bad total
44:
45:
                         1
                nmos
46:
47: 60 net-list ambiguities were resolved by random selection.
49: The net-lists failed to match.
50:
51:
                                 layout schematic
```

```
52:
                                     instances
 53:
             un-matched
                                     1
                                             1
 54:
             rewired
                                     30
                                             0
 55:
             size errors
                                     0
                                             0
 56:
             pruned
                                     0
                                             0
 57:
             active
                                     62
                                             62
 58:
             total
                                     62
                                             62
 59:
 60:
                                       nets
 61:
             un-matched
                                     32
                                             16
 62:
            merged
                                     15
                                             0
 63:
             pruned
                                     0
                                             0
                                             33
 64:
             active
                                     64
 65:
             total
                                     64
                                             33
 66:
 67:
                                     terminals
 68:
             un-matched
                                             1
 69:
            matched but
                                             0
70:
             different type
                                     0
71:
             total
                                     3
                                             3
72:
73:
74: Probe files from /qaia/class/student/komacd/CadDemo/LVS/schematic
75:
76: devbad.out:
77: I /IO<1>/NO
78: ? Device does not cross-match.
79:
80: netbad.out:
81: The no. of lines exceeded than specified by the variable lvsLimitLinesInOutFile.
82: To see the complete information please see the file:
 83: /qaia/class/student/komacd/CadDemo/LVS/schematic/netbad.out
 84:
 85: mergenet.out:
 86:
 87: termbad.out:
 88: T -1 osc out /osc out
 89: ? Terminal osc out in the schematic failed to match any terminal in the layout.
 90:
 91: prunenet.out:
 92:
 93: prunedev.out:
 94:
 95: audit.out:
 96:
 98: Probe files from /qaia/class/student/komacd/CadDemo/LVS/layout
99:
100: devbad.out:
101: I /+29
102: ? Device does not cross-match.
103:
```

\\qaia\Komacd\CadDemo\LVS\si.out


```
104: netbad.out:
105: The no. of lines exceeded than specified by the variable lvsLimitLinesInOutFile.
106: To see the complete information please see the file:
107: /gaia/class/student/komacd/CadDemo/LVS/layout/netbad.out
108:
109: mergenet.out:
110: The no. of lines exceeded than specified by the variable lvsLimitLinesInOutFile.
111: To see the complete information please see the file:
112: /gaia/class/student/komacd/CadDemo/LVS/layout/mergenet.out
113:
114: termbad.out:
115: The no. of lines exceeded than specified by the variable lvsLimitLinesInOutFile.
116: To see the complete information please see the file:
117: /qaia/class/student/komacd/CadDemo/LVS/layout/termbad.out
118:
119: prunenet.out:
120:
121: prunedev.out:
122:
123: audit.out:
124:
```

Post Layout-Simulation (Ring Oscillator):

Transient Response

Thu Apr 2 15:28:29 2020

Name Vis
/osc_out

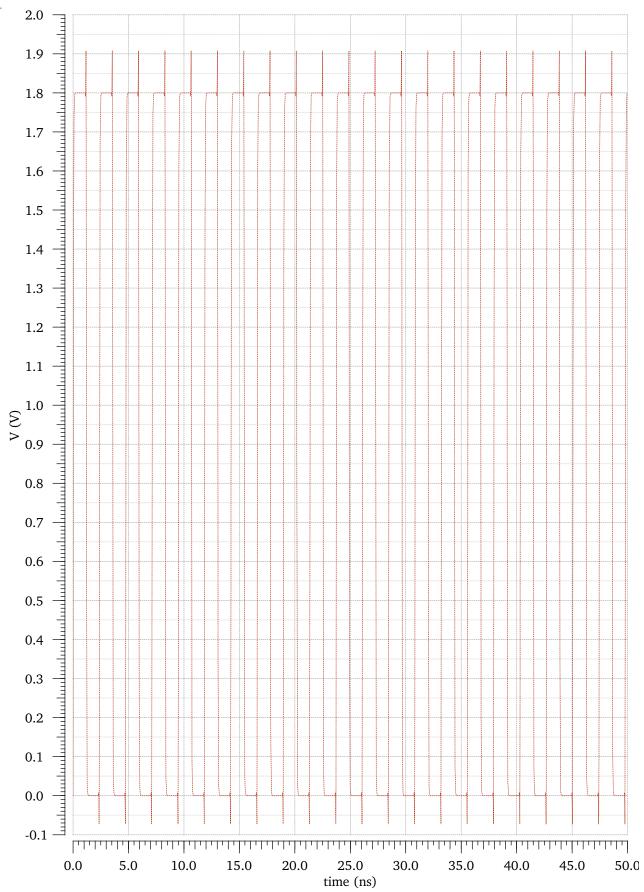

Conclusion:

S. No.	Description	Rise Time(us)	Fall Time(us)	Delay Time(us)
1.	Ring Oscillator	0.006us	0.005us	0us